

Name: Bryan Gonzalez
Date Submitted: 11/26/24

ID# 1001443032
Lab Section # 004

CSE 2441 – Digital Logic Design I

Fall Semester 2024

**Term Project – Eight-Bit, Two-Function Calculator
(100+ Points)**


Project Demonstration Deadline – December 3, 2024, 6:00 pm

Project Report Deadline – December 3, 2024, 11:59 pm


Early Submission Deadlines – November 26, 2024, 6:00 pm and 11:59 pm

This project is performed with the DE10-Lite and extension boards

Calculator top-level functional diagram

 

 Calculator top-level functional diagram (Quartus RTL)



List of added features

- Multiplexed Output Unit
- Blank Leading Zeros

Multiplexed Output Unit and Blank Leading Zeros Verilog

```
module OU_mplx(
    input CLK, Reset,
    input [7:0] TC,
    output [3:0] digit,
    output [0:6] SEG
);

    wire [7:0] SM;
    wire [3:0] sign, HUNDREDS, TENS, ONES;
    reg HUNDREDS_Blank, TENS_Blank;

    wire [1:0] SEL;
    wire [3:0] val;

    assign sign[0] = 1;
    assign sign[1] = ~TC[7];
    assign sign[2] = 1;
    assign sign[3] = 1;

    twos2signed t2s_inst(.A(TC), .B(SM));

    binary2bcd b2b_inst(
        .A(SM),
        .ONES(ONES),
        .TENS(TENS),
        .HUNDREDS(HUNDREDS)
    );

    Controller cont_inst(
        .CLK(CLK),
        .Reset(Reset),
        .SEL(SEL),
        .CAT(digit)
    );

    four2one f2o(
        .SEL(SEL),
        .digit0(ONES),
        .digit1({TENS_Blank ^ TENS[3],
                TENS_Blank ^ TENS[2],
                TENS_Blank ^ TENS[1],
                TENS_Blank ^ TENS[0]}),
        .digit2({HUNDREDS_Blank ^ HUNDREDS[3],
                HUNDREDS_Blank ^ HUNDREDS[2],
                HUNDREDS_Blank ^ HUNDREDS[1],
                HUNDREDS_Blank ^ HUNDREDS[0]}),
```

```

        .digit3(sign),
        .val(val)
    );

    //Checking for Leading zeroes
    always @ (TENS, HUNDREDS)
        if(HUNDREDS > 0)
            begin HUNDREDS_Blank=0; TENS_Blank = 0; end
        else if(TENS > 0)
            begin HUNDREDS_Blank=1; TENS_Blank = 0; end
        else
            begin HUNDREDS_Blank=1; TENS_Blank = 1; end

    bcd2seven_high bcd2sev_inst(
        val[3],val[2], val[1], val[0],
        SEG[0],
        SEG[1],
        SEG[2],
        SEG[3],
        SEG[4],
        SEG[5],
        SEG[6]
    );

endmodule

module four2one(
    input [1:0] SEL,
    input [3:0] digit0,
    input [3:0] digit1,
    input [3:0] digit2,
    input [3:0] digit3,
    output reg [3:0] val
);
    always @ (SEL)
        case ({SEL})
            2'b00: val = digit0;
            2'b01: val = digit1;
            2'b10: val = digit2;
            2'b11: val = digit3;
        endcase
endmodule

module Controller(
    input CLK, Reset,
    output [1:0] SEL,
    output [3:0] CAT

```

```

);
    wire slowclock;

    clock_div #(.DIV(100000)) keypad_clock_divider(
        .clk(CLK),
        .clk_out(slow_clock)
    );

    FSM fsm_inst(.slow_clock(slow_clock),.reset(Reset),.SEL(SEL),.CAT(CAT));
endmodule

module FSM(
    input slow_clock, reset,
    output reg [1:0] SEL,
    output reg [3:0] CAT
);
    reg [1:0] state, nextstate;
    always @ (negedge slow_clock, negedge reset)
        if (reset == 0) state <= 2'b0; else state <= nextstate;
    always @ (state)
        case ({state})
            2'b00: begin nextstate = 2'b01; SEL = 2'b00; CAT = 4'b1000; end
            2'b01: begin nextstate = 2'b10; SEL = 2'b01; CAT = 4'b0100; end
            2'b10: begin nextstate = 2'b11; SEL = 2'b10; CAT = 4'b0010; end
            2'b11: begin nextstate = 2'b00; SEL = 2'b11; CAT = 4'b0001; end
        endcase
endmodule

```

Top-level Verilog code

```
module Calculator(
    input CLK, CLR_Entry, CLR_All,
    input [3:0] row,
    output [3:0] col,
    output invalid,
    output OVR, ZERO,
    output [0:6] SEG,
    output [3:0] DIGIT
);

    wire CLK_IU;
    wire [3:0] val;
    wire [3:0] flags;
    wire [7:0] input_TC, output_TC, mux_TC;
    wire reset, trig, Load_A, Load_B, Load_R, add_sub, IUAU;

    CU CU_inst
    (
        .trig(~trig),                // input trig_sig
        .val(val),                  // input [3:0] val_sig
        .CLK_in(CLK),
        .CLK_out(CLK_IU),           // input CLK_sig
        .CLR_Entry(CLR_Entry),      // input CLR_Entry_sig
        .CLR_All(CLR_All),          // input CLR_All_sig
        .reset(reset),              // output reset_sig
        .Load_A(Load_A),            // output Load_A_sig
        .Load_B(Load_B),            // output Load_B_sig
        .Load_R(Load_R),            // output Load_R_sig
        .add_sub(add_sub),          // output add_sub_sig
        .IUAU(IUAU)                 // output IUAU_sig
    );

    IU IU_inst
    (
        .CLK(CLK_IU),               // input CLK_sig
        .RESET(reset),              // input RESET_sig
        .row(row),                  // input [3:0] row_sig
        .col(col),                  // output [3:0] col_sig
        .TC(input_TC),              // output [7:0] TC_sig
        .invalid(invalid),          // output invalid_sig
        .trig(trig),
        .value(val)
    );
```

```

OU_mplx OU_mplx_inst
(
    .CLK(CLK_IU) ,           // input CLK_sig
    .Reset(reset) ,          // input Reset_sig
    .TC(mux_TC) ,            // input [7:0] TC_sig
    .digit(DIGIT) ,          // output [3:0] digit_sig
    .SEG(SEG)                // output [0:6] SEG_sig
);

mux m
(
    .IUAU(IUAU),
    .input_TC(input_TC),
    .output_TC(output_TC),
    .mux_TC(mux_TC)
);

AU AU_inst
(
    .X(input_TC) ,           // input [7:0] x_sig
    .Ain(Load_A) ,           // input ain_sig
    .Bin(Load_B) ,           // input bin_sig
    .out(Load_R) ,           // input out_sig
    .clear(CLR_All) ,        // input clear_sig
    .add_sub(add_sub) ,      // input add_sub_sig
    .Result(output_TC) ,     // output [7:0] result_sig
    .Flags(flags)            // output [3:0] flags_sig
    //flag[3] = CARRY OUT
    //flag[2] = OVERFLOW
    //flag[1] = NEGATIVE
    //flag[0] = ZERO
);
assign ZERO = flags[0] & ~Load_R;
assign OVR = flags[2] & ~Load_R;

endmodule

module mux(
    input IUAU,
    input [7:0] input_TC, output_TC,
    output reg [7:0] mux_TC
);

    always @ (IUAU)
        if(IUAU == 0) mux_TC = input_TC;
        else mux_TC = output_TC;

endmodule

```



```

else nextstate <= S1;
end
else nextstate <= S1;
end
S2: begin if (trig) nextstate <= S3; else nextstate <= S2; end
S3: begin if (trig && val == 15) nextstate <= S4; else nextstate <=
S3; end
S4: nextstate <= S4;
endcase
end

always @ (state)
case(state)
S0: begin reset = 0 & CLR_All & CLR_Entry; Load_A = 1'b1;
Load_B = 1'b1; Load_R = 1'b1; IUAU = 0; end
S1: begin reset = 1'b1 & CLR_All & CLR_Entry; Load_A = 0;
Load_B = 1'b1; Load_R = 1'b1; IUAU = 0; end
S2: begin reset = trig & CLR_All & CLR_Entry; Load_A = 1'b1;
Load_B = 1'b1; Load_R = 1'b1; IUAU = 0; end
S3: begin reset = 1'b1 & CLR_All & CLR_Entry; Load_A = 1'b1;
Load_B = 0; Load_R = 1'b1; IUAU = 0; end
S4: begin reset = 1'b1 & CLR_All & CLR_Entry; Load_A = 1'b1;
Load_B = 1'b1; Load_R = 0; IUAU = 1'b1; end
endcase
endmodule


```


Test demo. Must include specified requirements and added features.

- Testing normal calculation
 - a. $34+75$
 - b. $34-75$
 - c. $-34+75$
 - d. $-34-74$
 - e. $127+9$
 - f. $127-9$
 - g. $9+9$
 - h. $9-9$
 - i. $86-125$
 - j. $86+125$
- Testing multiplexed display
- Testing blank leading zeroes
 - a. Single digit
 - b. Two digits
 - c. Negative single digit
 - d. Negative two digit

I was going to submit pictures to show my tests for the report but because of how the multiplexed display works, the camera on my phone can only capture two or three digits displaying at one time.

Here is my attempt to capture -123

 

 

It may be inconvenient but cool to see how the multiplexed display is working. We get to see the FSM selecting cycling across all the digits, displaying “one at a time”. (Note our camera does capture the digit before and after the selected digit to display.)

The TA, Andrew did see the multiplex display working properly and blank leading zeroes.

Table of results

A	Op	B	Result	Flag
34	+	75	109	---
34	-	75	-41	---
-34	+	75	41	---
-34	-	75	-109	---
127	+	9	-120	OVR
127	-	9	118	---
9	+	9	18	---
9	-	9	0	ZERO
86	-	125	-39	---
86	+	125	-45	OVR

Description of unresolved problems if any

I don't feel like I have any unresolved problems. I am satisfied with my term project and got all the extra credit features to work.

Lessons learned

I came into the course knowing a little about digital logic already and now I feel like I really have a grasp of how it works and some possible applications of it in the real world such as a calculator. We I hadn't had any experience with was sequential circuits. I learned how sequential circuits can be used to create memory in the form of registers or to hold states. I feel like I can apply what I learned in Computer Theory like DFA's and I can apply that to designing sequential circuits. Also working with bits and different number systems, I feel a lot more comfortable working with binary, two's complement, hexadecimal and conversions to decimal. Lastly, I learned about verilog and we can use to program an FPGA.